
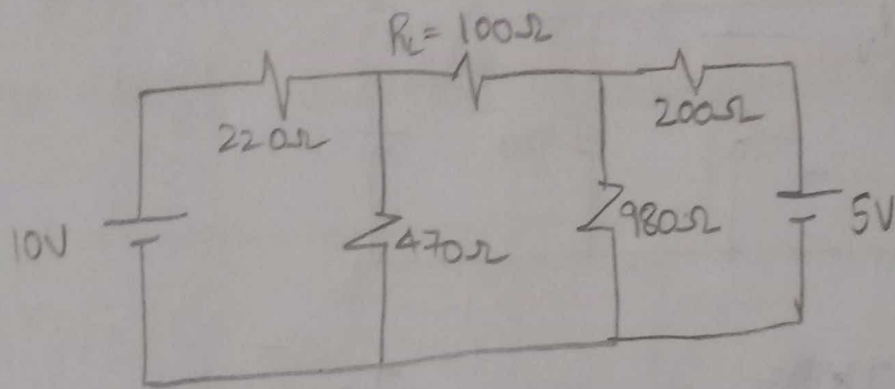


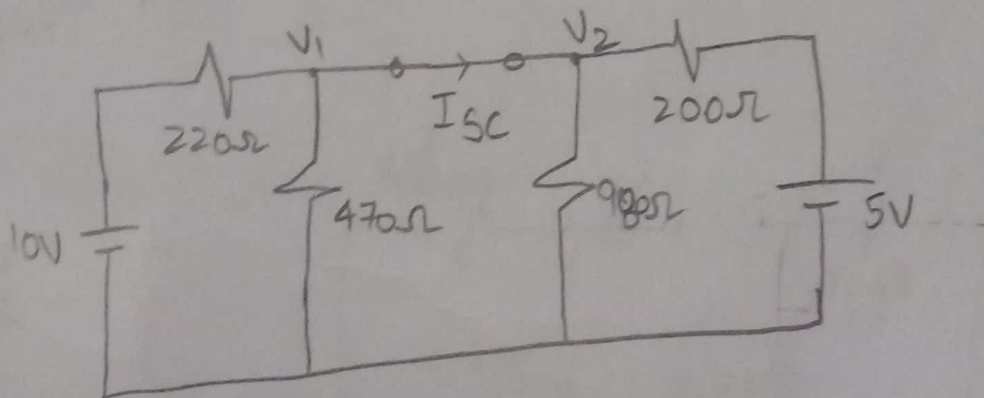
7. Obtain the Norton's model for the given circuit.



Sol



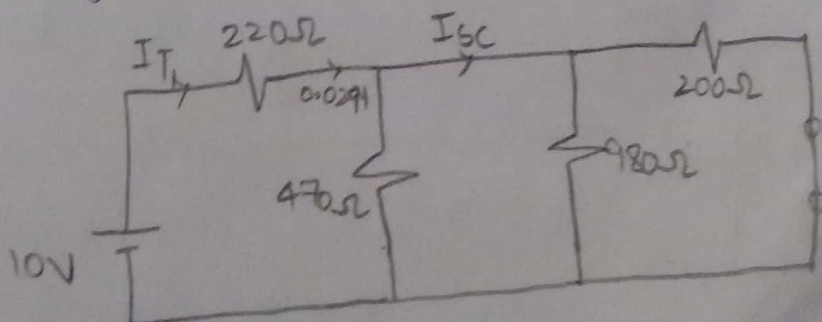(case i) while 10V source is acting alone



$$R_T = \frac{200 \times 980}{1480} = 166.1 \Omega$$


$$= \frac{470 \times 166.1}{166.1} = 122.7 \Omega$$

$$R_T = 122.7 + 220 = 342.7 \Omega$$


$$I_{T_1} = \frac{V}{R_T} = \frac{10}{342.7} = 0.0291 A$$

$$I_{SC_1} = \frac{0.0291 \cdot 470}{470 + 166.1}$$

$$I_{SC_1} = 0.021 A$$


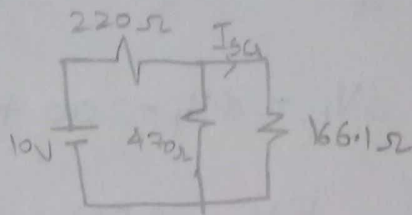


Case 2) while 5V sources acting alone

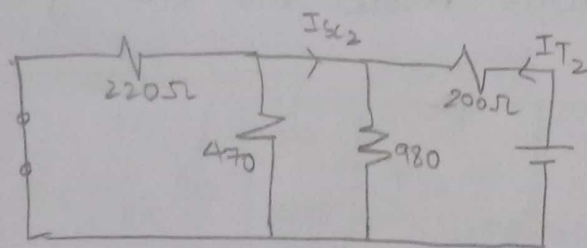


$$I_{SC_2} = I_{T_2} \times \frac{980}{980 + 220 + 470}$$

$$I_{SC} = I_{SC_1} - I_{SC_2}$$

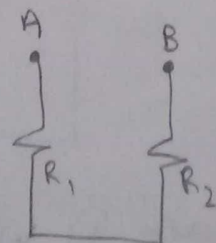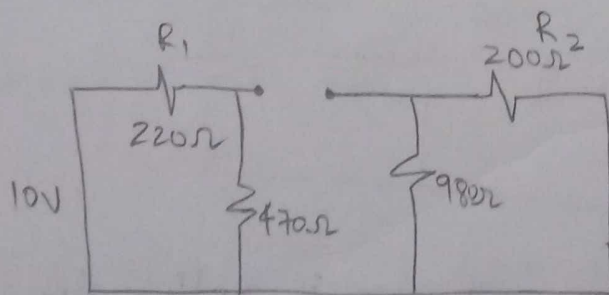

$$R_{eq} = R_1 + R_2$$

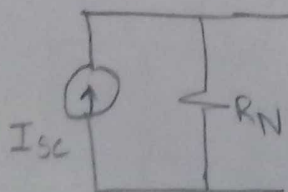

Determine the average, RMS, form factor and peak factor of sign voltage waveform

sol Form factor = $\frac{V_{rms}}{V_{avg}} = \frac{V_m/\sqrt{2}}{\frac{2V_m}{\pi}} = \frac{V_m}{\sqrt{2}} \times \frac{\pi}{2V_m}$

$$\Rightarrow \frac{1}{\sqrt{2}} \times \frac{\pi}{2} = \frac{\pi}{2\sqrt{2}} = 1.11$$

$$\boxed{\text{Form Factor} = 1.11}$$

$$\text{Peak Factor} = \frac{V_m}{V_{rms}} = \frac{V_m}{V_m/\sqrt{2}} = \frac{V_m}{1} \times \frac{\sqrt{2}}{V_m}$$

$$\boxed{\text{Peak factor} = 1.414}$$

VAverage of Sine wave form

$$* \frac{1}{\pi} \int_0^{\pi} V_m \sin t \, dt$$

$$= \frac{V_m}{\pi} [-\cos t]_0^{\pi}$$

$$= -\frac{V_m}{\pi} [-1 - 1]$$

$$= \frac{2V_m}{\pi} = \boxed{\frac{2V_m}{\pi} = V_{avg}}$$

$$* \sqrt{\frac{1}{2\pi} \int_0^{2\pi} (V_m \sin t)^2 \, dt}$$

$$= \sqrt{\frac{V_m^2}{2\pi} \int_0^{2\pi} \left[\frac{1 - \cos 2t}{2} \right] \, dt}$$

$$= \sqrt{\frac{V_m^2}{4\pi} \left[t - \frac{\sin 2t}{2} \right]_0^{2\pi}}$$

$$= \sqrt{\frac{V_m^2}{4\pi} \left[\left(2\pi - \frac{\sin 4\pi}{2} \right) - \left(0 - \frac{\sin 0}{2} \right) \right]}$$

$$\sin t =$$

$$\therefore \cos 2t$$

$$\therefore \sin 2t$$

$$= \sqrt{\frac{V_m^2}{4\pi^2} \left[\frac{2\pi}{1} - \frac{\sin 4\pi}{2} \right]}$$

$$= \sqrt{\frac{V_m^2}{2} \left[1 - \frac{0}{2} \right]}$$

$$= \sqrt{\frac{V_m^2}{2}} = \frac{V_m}{\sqrt{2}}$$

$$\boxed{V_{rms} = \frac{V_m}{\sqrt{2}}} \quad ***$$

2) ^{*} Voltage and current for a circuit with two elements in series are expressed as follows.

$$V(t) = 170 \sin(6280t + \pi/3) \text{ volts.}$$

$$i(t) = 8.5 \sin(6280t + \pi/2) \text{ Amperes.}$$

Determine the frequency in Hz, power factor, nature and values of the elements.


A)

$$\text{Power factor} = \cos 30^\circ$$

$$= \sqrt{3}/2$$

$$= 0.82 \text{ leading}$$

Power factor

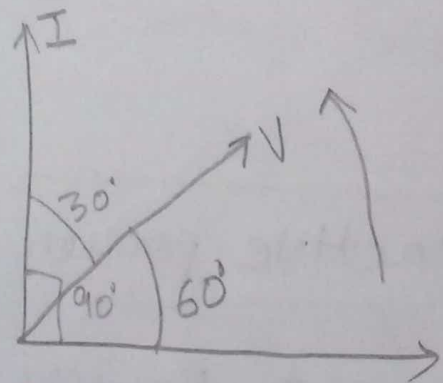

$$\omega = 2\pi f = 6280$$

$$= 2\pi \cancel{100} f = 6280$$

$$f = 999 \text{ Hz}$$

As current is leading the voltage by 30° , circuit elements are having resistive & capacitive nature.

$$Z = \frac{V_m \angle 60^\circ}{I_m \angle 90^\circ} = \frac{170^\circ}{18.5} \angle -30^\circ$$

$$Z = 20 \angle -30^\circ \rightarrow \text{polar form}$$

$$Z = 20 \cos 30^\circ - j 20 \sin 30^\circ$$

$$\boxed{Z = 17.7 - j10} \Omega$$

\swarrow R \swarrow $-jX_C$

$$R = 17.7 \Omega$$

$$X_C = \frac{10}{\omega C} = \frac{1}{\omega C}$$

$$C = \frac{1}{10\omega} = \frac{1}{10(6280)}$$

$$C = 15.9 \times 10^{-6}$$

$$\boxed{C = 15.9 \mu F}$$

$$\text{Power} = \frac{V_m}{\sqrt{2}} \cdot \frac{I_m}{\sqrt{2}} \cdot \cos \theta$$

$$Q = VI \sin \theta$$

$$V(t) = 27 \sin 340t$$


$$i(t) = 5 \sin (340t + \pi/6)$$

$+\pi/2$
Pure
capacitor


$-\pi/2$
Pure
Inductor

$-\pi/6$
 R_L

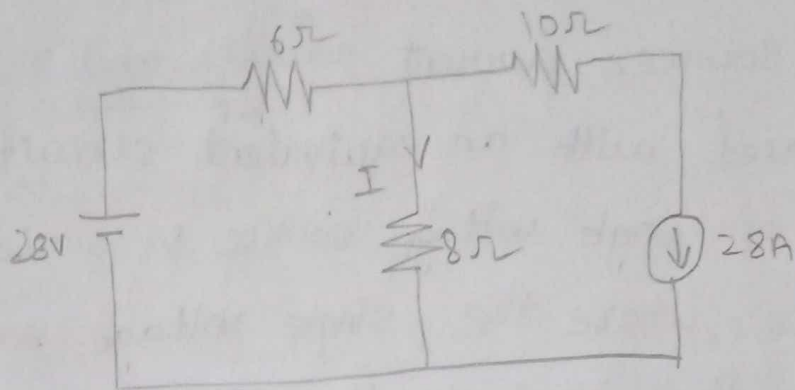3. Determine the current in 8Ω resistor using superposition theorem.




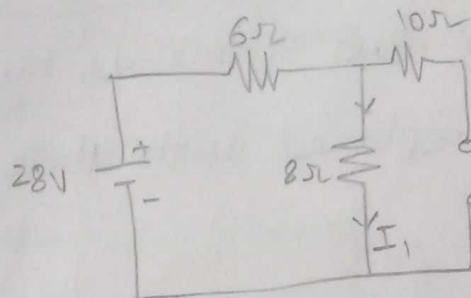Sol: Case 1) while 28V source acting alone



$$I_1 = \frac{28}{6+8} = 2A$$

Case 2) while 28A source acting alone

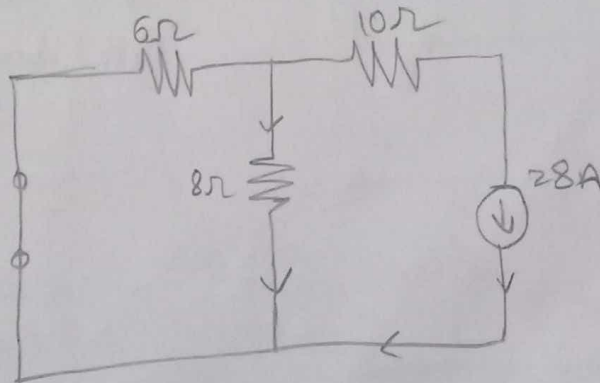

$$I_2 = \frac{-28 \cdot 6}{6+8}$$

$$I_2 = -12A$$

$$I_{8\Omega} = 2 - 12 = -10A$$