



R18 Regulation

TKR COLLEGE OF ENGINEERING AND TECHNOLOGY

(Autonomous, Accredited by NAAC with 'A' Grade)

Subject code: 2E1AD

B.Tech I Year I Semester Examinations, December 2019

BASIC ELECTRICAL ENGINEERING

(Common to CE,EEE,ME & IT)

Maximum Marks: 70

Date: 23.12.2019 Duration: 3 hours

- Note:
1. This question paper contains two parts A and B.
 2. Part A is compulsory which carries 20 marks. Answer all questions in Part A.
 3. Part B consists of 5 Units. Answer any one full question from each unit.
 4. Each question carries 10 marks and may have a, b, c, d as sub questions.

Part-A

All the following questions carry equal marks

(10x2M=20 Marks)


- 1 Two resistances of $4\ \Omega$ and $6\ \Omega$ are connected in parallel across 10V battery. Determine the current through $6\ \Omega$ resistance.
- 2 State Kirchhoff current and voltage laws
- 3 Define peak and form factor.
- 4 Three inductive coils each with resistance of $15\ \Omega$ and an inductance of $0.03\ \text{H}$ are connected in star to 3 phases 400V, 50 Hz supply. Calculate the phase voltages
- 5 State reciprocity theorem.
- 6 What is the condition for Maximum power transfer in DC circuits?
- 7 A DC generator supplies load of 10 KW at 220V through feeders of resistance $0.1\ \Omega$. The resistances of armature and shunt field windings is $0.05\ \Omega$ and $100\ \Omega$ respectively. Calculate the terminal voltage
- 8 In a single phase transformer $N_p=350$ Turns, $N_s = 1050$ Turns and $E_p= 400\ \text{V}$. Find E_s
- 9 Define power factor and list out the methods for power factor improvement.
- 10 What is the function of MCCB?

Part-B

Answer All the following questions.

(10M X 5=50Marks)

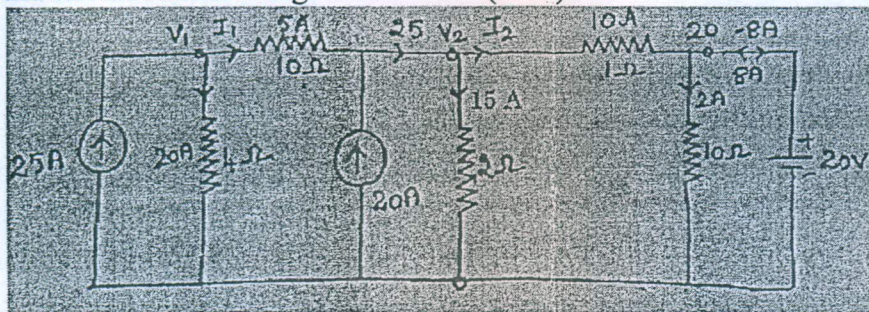- 11 Using nodal analysis find the node voltages and the currents through all the resistors for the circuit shown in fig. (10M)



OR

- 12 i) Explain the various types of magnetic materials. (5M)
ii) Derive the expressions for Mutual inductance. (5M)




- 13 Derive the expressions for single phase RLC series and RLC parallel circuits. (10M)

OR


- 14 Three equal impedances each of $8+j10\ \Omega$ are connected in star. This is further connected to 440V, 50 Hz three phase supply. Calculate the active power, reactive power, line currents and phase currents. (10M)

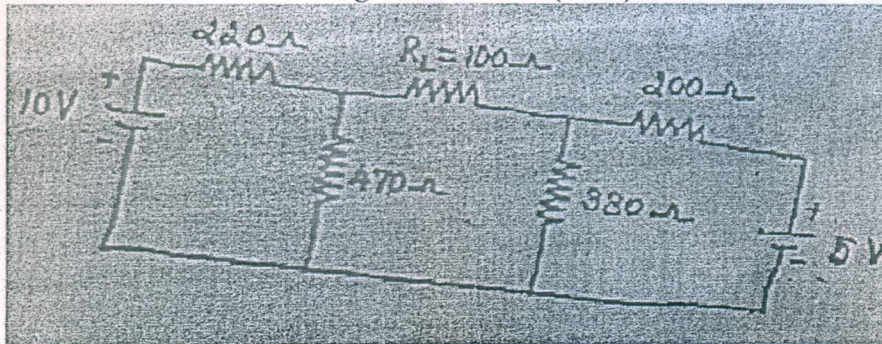- 15 Obtain the Norton's model for the given circuit. (10M)



OR

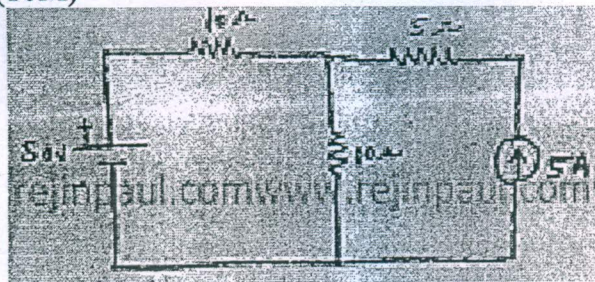- 16 Find the current through various branches of the circuit shown below by employing superposition theorem. (10M)



- 17 With a neat diagram explain the construction and principle of operation of single phase transformer. What are the characteristics of an ideal transformer? (10M)

OR

- 18 Derive the EMF and Torque equation of a DC Motor. (10M)

- 19 Explain in detail about various types of batteries used for electrical applications. (10M)

OR

- 20 Explain in detail about MCB and ELCB with neat diagram. (10M)