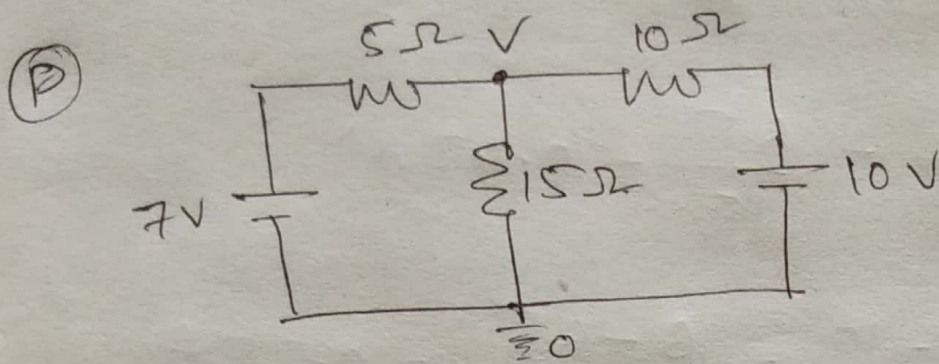


Nodal Analysis for one unknown Voltage:-



→ The point at which two or more resistors are connected that point is called node.

→ Apply Kcl + ohm's law for nodal Analysis.

→ Now, Apply Kcl at node, [we consider V is the higher than 7V & 10V]

$$\frac{V-7}{5} + \frac{V-10}{10} + \frac{V-0}{15} = 0$$

$$V \left[\frac{1}{5} + \frac{1}{10} + \frac{1}{15} \right] = \frac{7}{5} + 1 = \frac{12}{5}$$

$$V \left[\frac{6+3+2}{30} \right] = \frac{12}{5}$$

$$V \left[\frac{11}{30} \right] = \frac{12}{5}$$

$$V = 6.5V$$

$$I_{5\Omega} = \frac{V-7}{5} = \frac{7-6.5}{5} = 0.1 \text{ A}$$


$$I_{15\Omega} = \frac{V}{15} = \frac{6.5}{15} = 0.43 \text{ A}$$

$$I_{10\Omega} = \frac{V-10}{10} = \frac{10-6.5}{10} = 0.35 \text{ A}$$

$$\therefore I_{5\Omega} + I_{10\Omega} = I_{15\Omega}$$

$$0.1 + 0.35 = 0.45 \text{ A}$$

Nodal Analysis for two unknown voltages:

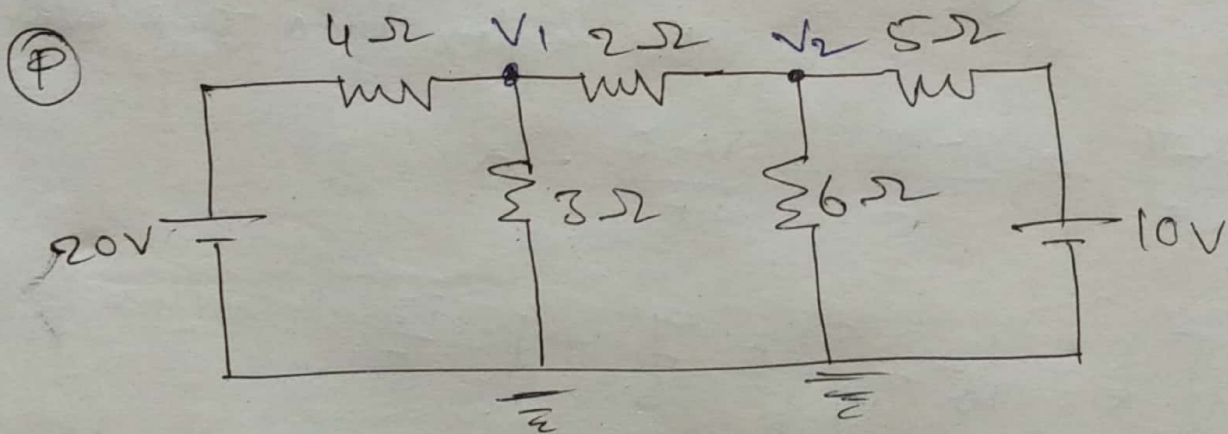

Apply Kcl at node ①

$$\frac{V_1 - 20}{4} + \frac{V_1}{3} + \frac{V_1 - V_2}{2} = 0$$

$$V_1 \left[\frac{1}{4} + \frac{1}{3} + \frac{1}{2} \right] - 0.5V_2 = 5$$

$$1.08V_1 - 0.5V_2 = 5 \quad \text{--- (1)}$$


Apply Kcl at node (2)

$$\frac{V_2 - V_1}{2} + \frac{V_2}{6} + \frac{V_2 - 10}{5} = 0$$

$$V_1 \left[-\frac{1}{2} \right] + V_2 \left[\frac{1}{2} + \frac{1}{6} + \frac{1}{5} \right] = 2 \quad \text{--- (2)}$$

$$V_1 = 2.79V, \quad V_2 = 3.95V$$

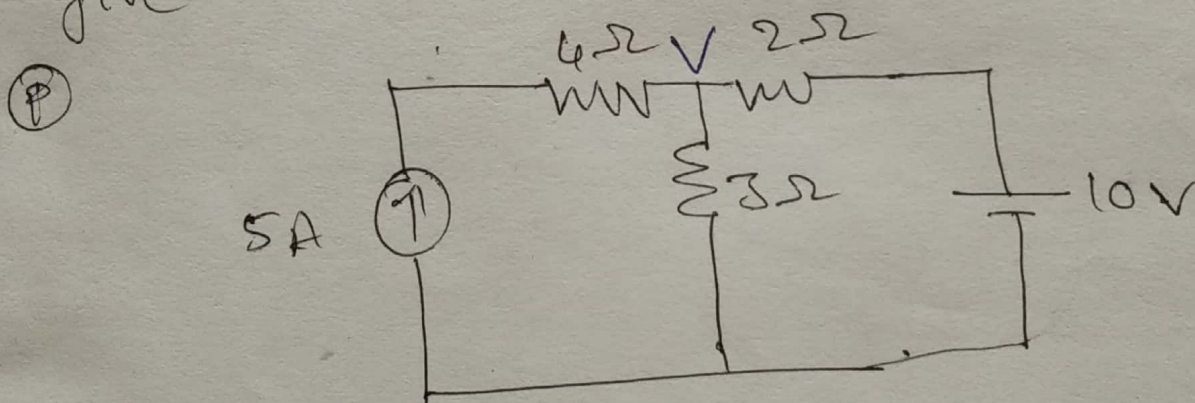Nodal Analysis when current source is given



Solⁿ:- Apply Kcl + Ohm's law

$$\frac{V - 10}{2} + \frac{V}{3} = 5$$

$$0.5V + 0.33V = 10$$

$$0.83V = 10$$

$$V = \frac{10}{0.83} = 12V$$


$$I_{2\Omega} = \frac{12-10}{2} = 1A$$

$$I_{3\Omega} = \frac{V}{3} = \frac{12}{3} = 4A$$

$$I_{2\Omega} + I_{3\Omega} = 1 + 4 = 5A$$

Star - Delta transformation Technique:-

Star:-

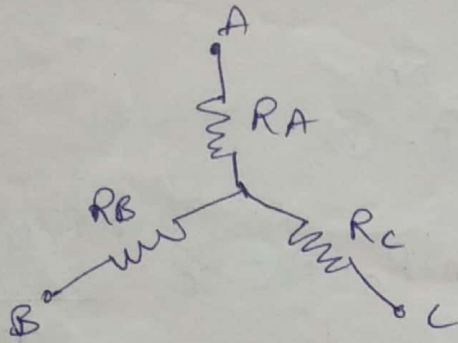


$$R_{AB}(Y) = R_A + R_B$$

$$R_{BC}(Y) = R_B + R_C$$

$$R_{CA}(Y) = R_C + R_A$$

Delta:-

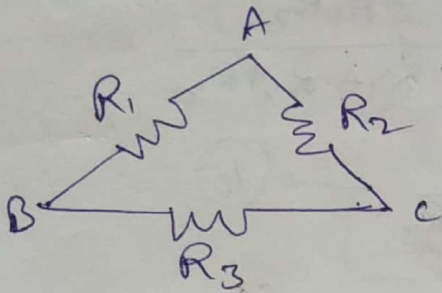

$$R_{AB}(\Delta) = R_1 \parallel (R_2 + R_3)$$

$$R_{AB}(\Delta) = \frac{R_1 R_2 + R_1 R_3}{R_1 + R_2 + R_3}$$

$$R_{BC}(\Delta) = R_3 \parallel (R_2 + R_1)$$

$$R_{BC}(\Delta) = \frac{R_1 R_3 + R_2 R_3}{R_1 + R_2 + R_3}$$

$$R_{CA}(\Delta) = R_2 \parallel (R_1 + R_3)$$

$$= \frac{R_1 R_2 + R_2 R_3}{R_1 + R_2 + R_3}$$

Now, Equate the Y & Δ


$$R_{AB}(Y) = R_{AB}(\Delta)$$

$$R_A + R_B = \frac{R_1 R_2 + R_1 R_3}{R_1 + R_2 + R_3} \quad \text{--- ①}$$

$$R_B + R_C = \frac{R_1 R_3 + R_2 R_3}{R_1 + R_2 + R_3} \quad \text{--- ②}$$

$$R_C + R_A = \frac{R_1 R_2 + R_2 R_3}{R_1 + R_2 + R_3} \quad \text{--- ③}$$

To get relation b/w Δ to Y

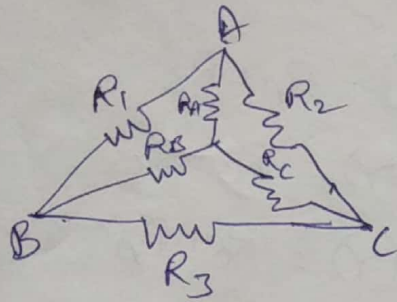

to get R_A
eqn ① + ③ - ②

$$R_A + \cancel{R_B} + \cancel{R_A} + \cancel{R_C} - \cancel{R_B} - \cancel{R_C} = \frac{R_1 R_2 + R_1 R_3 + R_2 R_3 - R_1 R_3 - R_2 R_3}{R_1 + R_2 + R_3}$$

$$2R_A = \frac{2R_1 R_2}{R_1 + R_2 + R_3}$$

$$\therefore \boxed{R_A = \frac{R_1 R_2}{R_1 + R_2 + R_3}} \quad \text{--- (4)}$$

to get R_B

\therefore eqn ① + ② - ③

$$\cancel{R_A} + \cancel{R_B} + R_B + \cancel{R_C} - \cancel{R_A} - \cancel{R_C} = \frac{R_1 R_2 + R_1 R_3 + R_1 R_3 + R_2 R_3 - R_1 R_2 - R_2 R_3}{R_1 + R_2 + R_3}$$

$$2R_B = \frac{2R_1 R_3}{R_1 + R_2 + R_3}$$

$$\boxed{R_B = \frac{R_1 R_3}{R_1 + R_2 + R_3}} \quad \text{--- (5)}$$

to get R_C


\therefore eqn ② + ③ - ①

$$\cancel{R_A} + \cancel{R_C} + \cancel{R_B} + R_C - \cancel{R_A} - \cancel{R_B} = \frac{R_1 R_3 + R_2 R_3 + R_1 R_2 + R_2 R_3 - R_1 R_2 - R_1 R_3}{R_1 + R_2 + R_3}$$

$$2R_C = \frac{2R_2 R_3}{R_1 + R_2 + R_3}$$

$$\boxed{R_C = \frac{R_2 R_3}{R_1 + R_2 + R_3}} \quad \text{--- (6)}$$

The relation b/w γ to Δ :-

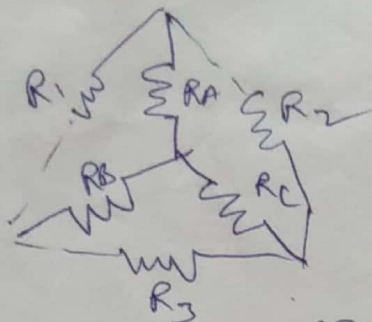

$$R_A R_B + R_B R_C + R_C R_A = \left(\frac{R_1 R_2}{R_1 + R_2 + R_3} \right) \left(\frac{R_1 R_3}{R_1 + R_2 + R_3} \right) + \left(\frac{R_1 R_3}{R_1 + R_2 + R_3} \right) \left(\frac{R_2 R_3}{R_1 + R_2 + R_3} \right) + \left(\frac{R_2 R_3}{R_1 + R_2 + R_3} \right) \left(\frac{R_1 R_2}{R_1 + R_2 + R_3} \right)$$

$$= \frac{R_1^2 R_2 R_3}{(R_1 + R_2 + R_3)^2} + \frac{R_1 R_2 R_3^2}{(R_1 + R_2 + R_3)^2} + \frac{R_1 R_2^2 R_3}{(R_1 + R_2 + R_3)^2}$$

$$= \frac{R_1 R_2 R_3 [R_1 + R_2 + R_3]}{(R_1 + R_2 + R_3)^2}$$

$$R_A R_B + R_B R_C + R_C R_A = \frac{R_1 R_2 R_3}{R_1 + R_2 + R_3}$$

$$R_A R_B + R_B R_C + R_C R_A = R_1 R_C$$

$$\therefore R_1 = \frac{R_A R_B + R_B R_C + R_C R_A}{R_C}$$


Similarly

$$R_2 = \frac{R_A R_B + R_B R_C + R_C R_A}{R_B}$$


$$R_3 = \frac{R_A R_B + R_B R_C + R_C R_A}{R_A}$$

Star - delta transformation technique


Star:-

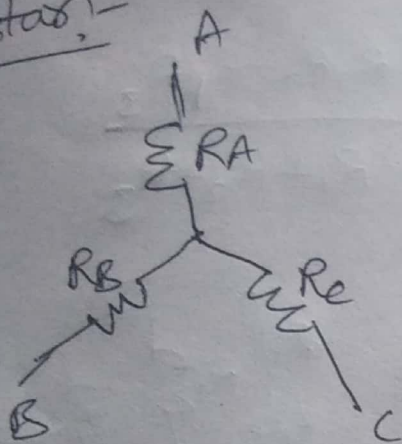



$$R_{AB}(Y) = R_A + R_B$$

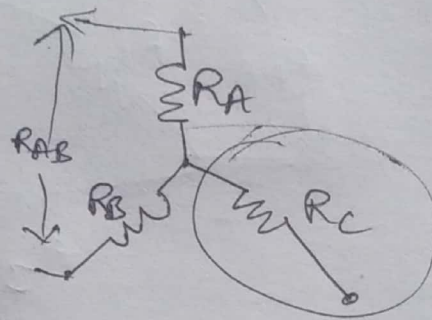



\Rightarrow

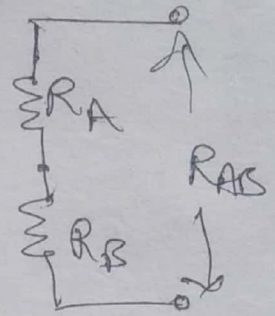


$$R_{BC}(Y) = R_B + R_C$$

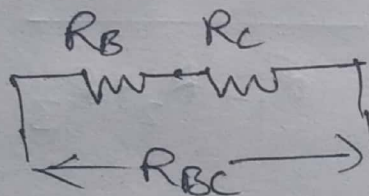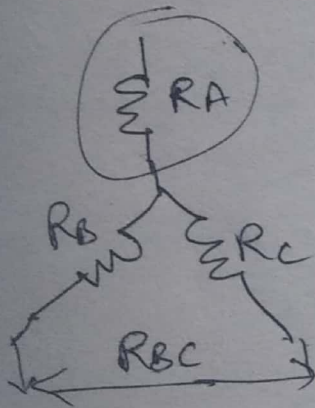

$$R_{CA}(Y) = R_C + R_A$$

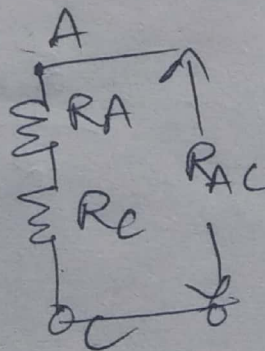
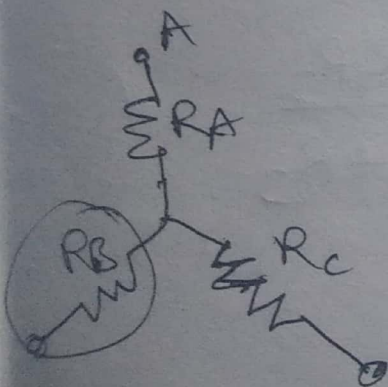


Delta:-

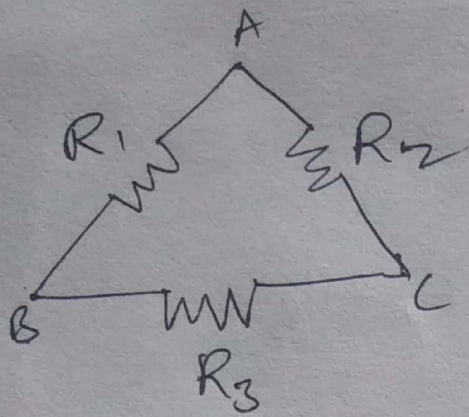


$$R_{AB}(\Delta) = R_1 // (R_2 + R_3)$$
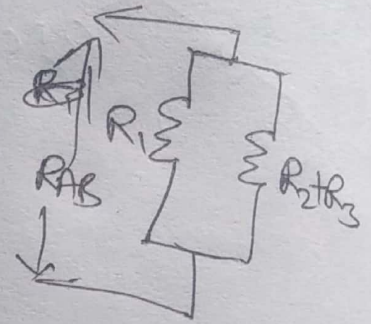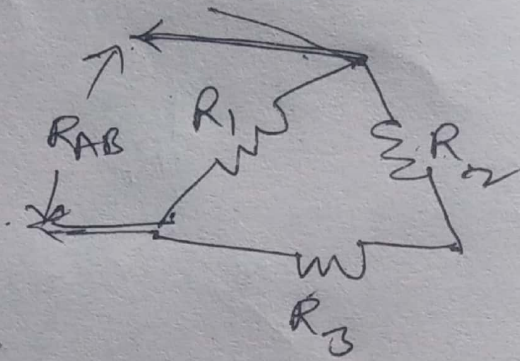
$$= \frac{R_1 R_2 + R_1 R_3}{R_1 + R_2 + R_3}$$




$$R_{BC}(\Delta) = R_3 // (R_1 + R_2)$$

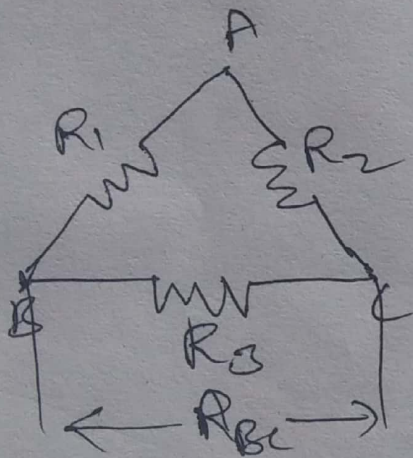

$$= \frac{R_3 R_1 + R_2 R_3}{R_1 + R_2 + R_3}$$

$$R_{CA}(\Delta) = R_2 // (R_1 + R_3)$$

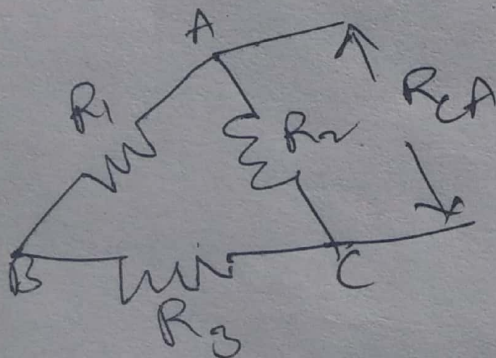


$$= \frac{R_1 R_2 + R_2 R_3}{R_1 + R_2 + R_3}$$

→ Q1 $R_1 = R_2 = R_3 = R,$

$$R_A = \frac{R}{3R} = \frac{R}{3} \Rightarrow \boxed{R_A = \frac{R}{3}}$$


Problem

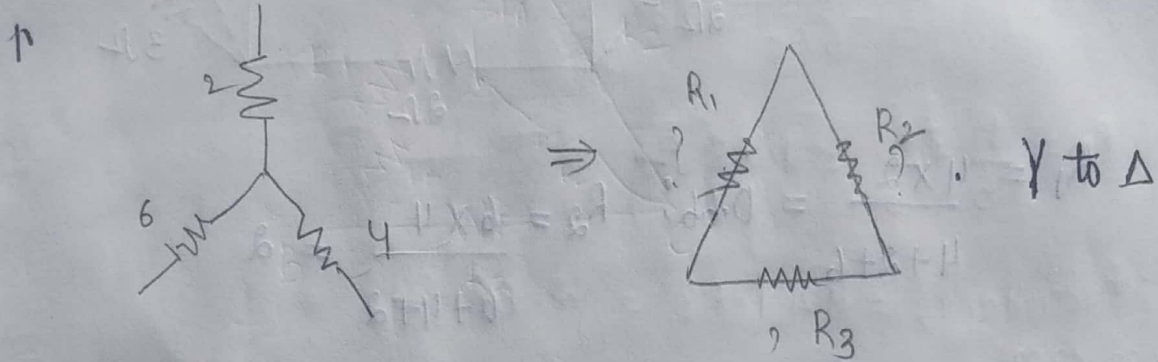

Ans: $R_1 = 6 + 2 + \frac{6 \times 2}{4} = 11$

$$R_2 = 2 + 4 + \frac{2 \times 4}{6} = 7.3$$
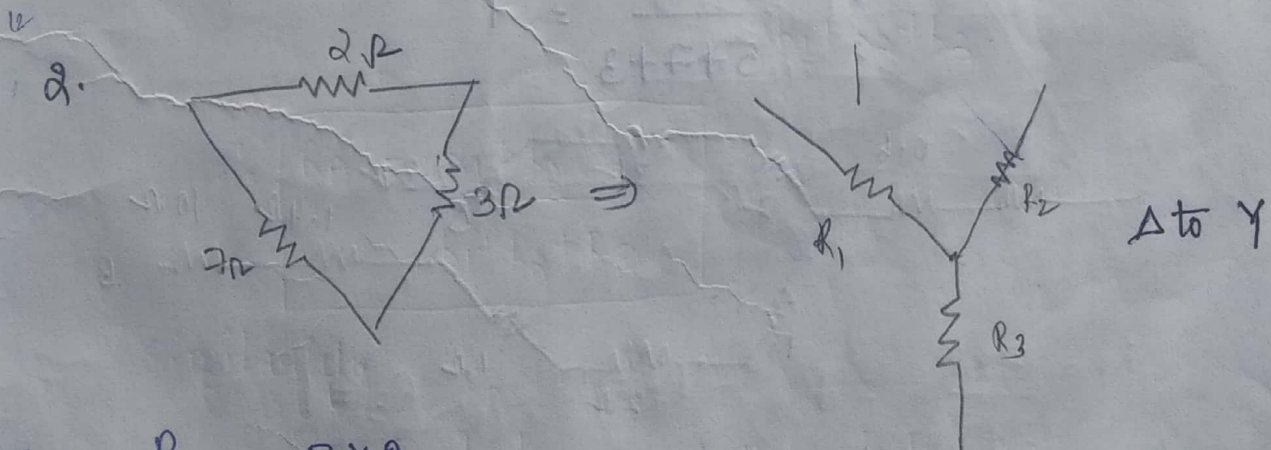
$$R_3 = 6 + 4 + \frac{6 \times 4}{2} = 22$$




Ans: $R_1 = \frac{7 \times 2}{7 + 2 + 3} = 1.1$

$$R_3 = \frac{7 \times 3}{2 + 3 + 7} = 1.7$$

$$R_2 = \frac{2 \times 3}{2 + 3 + 7} = 0.5 \Omega$$

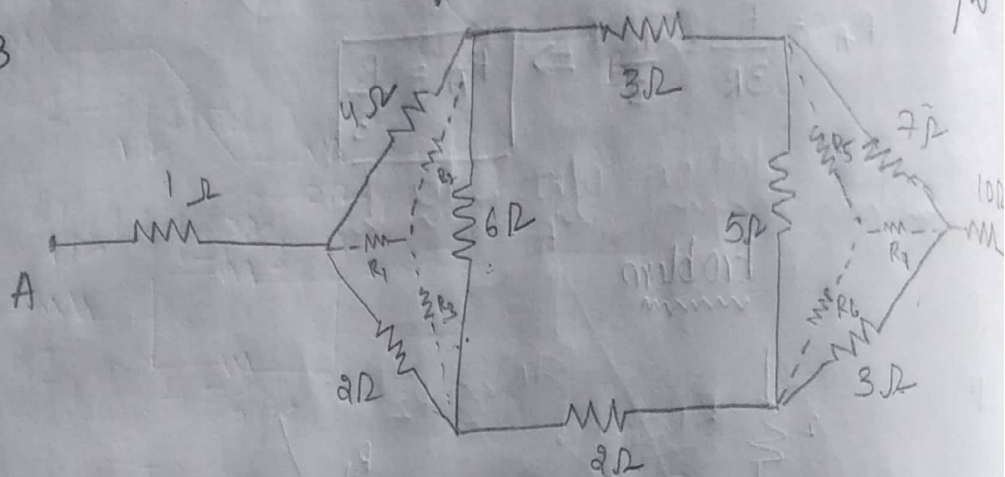3. For the circuit shown Fig find the resistance b/w A & B





Ans:

$$R_1 = \frac{4 \times 2}{4 + 2 + 6} = 0.66, \quad R_2 = \frac{6 \times 4}{6 + 4 + 2} = 2$$

$$R_3 = \frac{6 \times 2}{6 + 2 + 4} = 1$$


$$R_4 = \frac{7 \times 3}{7 + 3 + 5} = 1.4, \quad R_5 = \frac{5 \times 7}{5 + 7 + 3} = 2.33$$
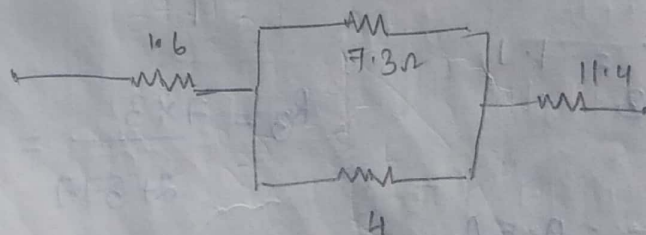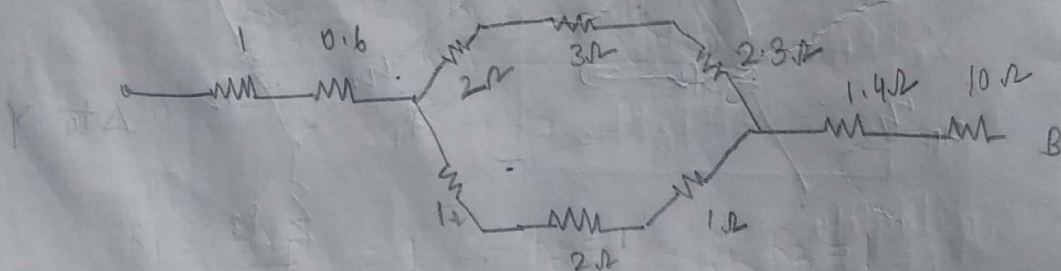
$$R_6 = \frac{5 \times 3}{5 + 7 + 3} = 1$$



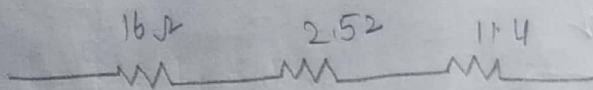7.3 & 4 are parallel


$$R_a = \frac{7.3 \times 4}{7.3 + 4} = 2.59$$





$$R_{\text{resultant}} = 16 + 2.5 + 11.4$$



$$= 15.59\Omega$$

4. For circuit shown in Fig

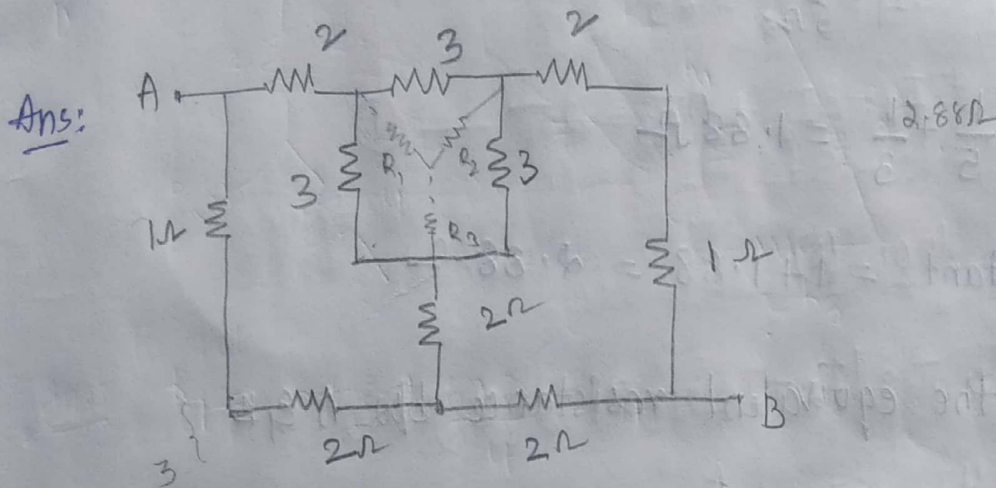
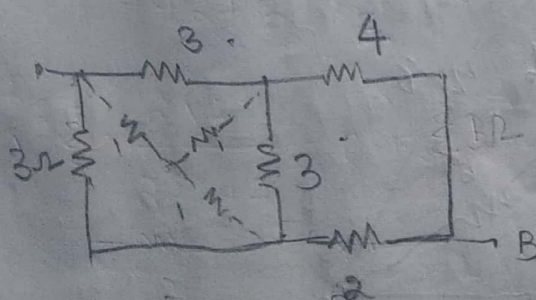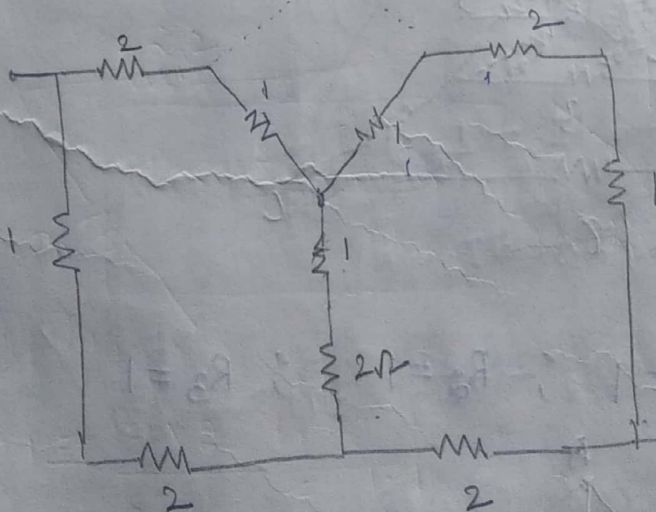
$$R_1 = \frac{3 \times 3}{3 + 3 + 3} = \frac{9}{9} = 1 \quad ; \quad R_2 = \frac{3 \times 3}{3 + 3 + 3} = 1 \quad , \quad R_3 = \frac{3 \times 3}{3 + 3 + 3} = 1$$



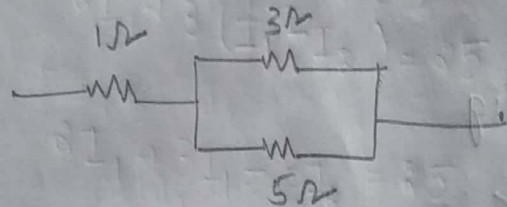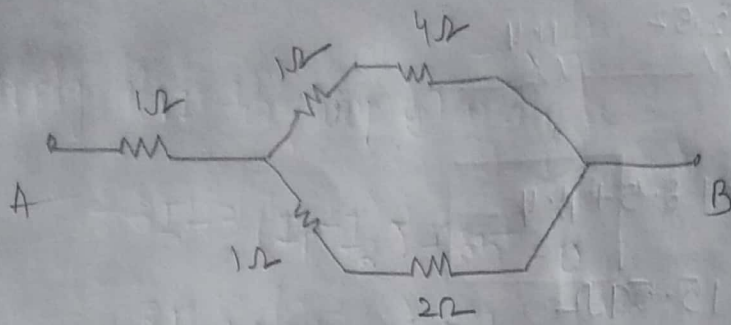


$$R_p = \frac{1}{\frac{1}{3} + \frac{1}{5}} = 1.88 \Omega$$


$$R_{\text{resultant}} = 1 + 1.88 = 2.88 \Omega$$

5. Obtain the equivalent resistance b/w A & B

Ans


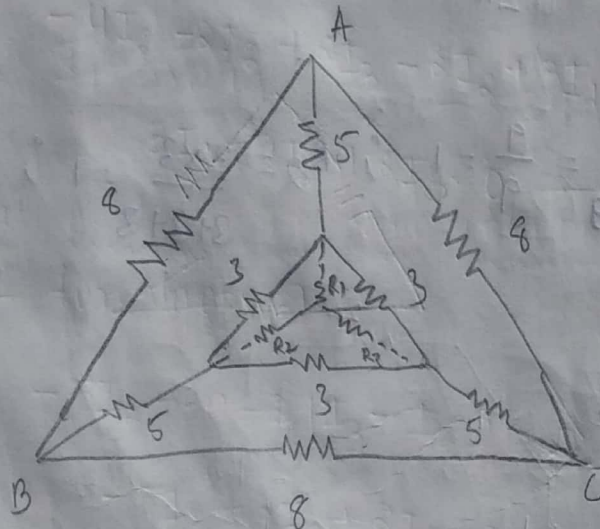

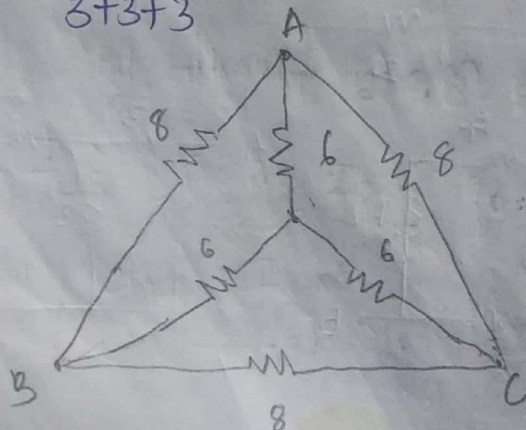
$$R_1 = \frac{3 \times 3}{3+3+3} = 1; \quad R_2 = 1; \quad R_3 = 1$$




8 & 6 are in parallel
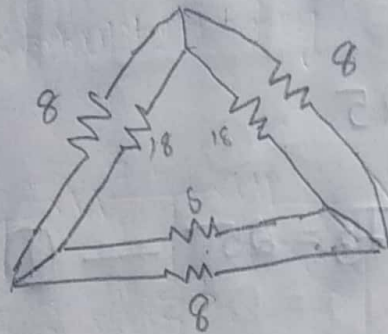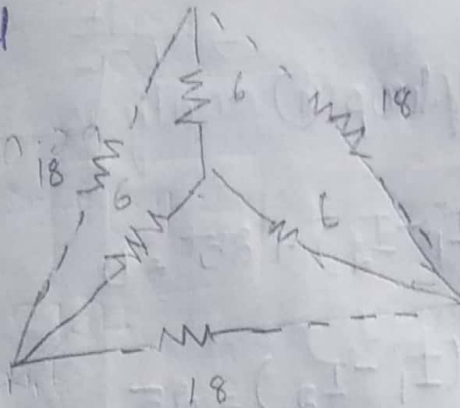
$$R = \frac{1}{\frac{1}{8} + \frac{1}{6}} = 3.42$$



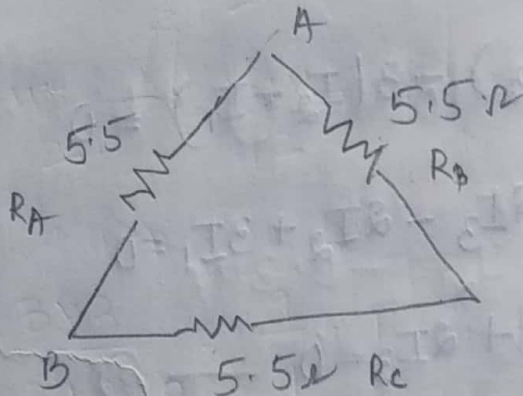8 & 18 are in parallel so $\Rightarrow \frac{18 \times 8}{18 + 8} = 5.5 \Omega$



$$R_{AB} = R_A \parallel (R_B + R_C)$$

$$= \frac{5.5(5.5 + 5.5)}{5.5 + 5.5 + 5.5} = \frac{5.5 \times 11}{16.5} = 3.7 \Omega$$

$$R_{BC} = 3.7 \Omega, R_{CA} = 3.7 \Omega$$