
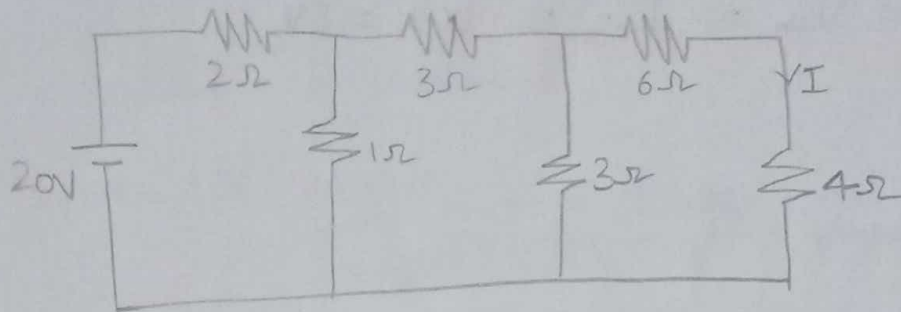


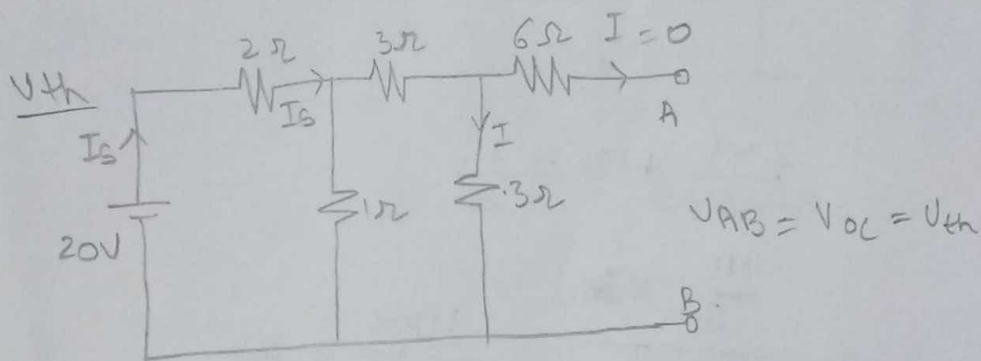4. Find current flowing through 4Ω resistor for the circuit shown in below figure using Thevenin's Theorem.



Sol



Applying KCL • Method-1

$$\frac{V-20}{2} + \frac{V}{6} + \frac{V}{1} = 0$$

$$3V - 60 + V + 6V = 0$$

$$10V = 60$$

$$V = 6V //$$

$$I = \frac{V}{6} = \frac{6}{6} = 1A //$$

Method-2

$$\frac{6 \times 1}{7} = \frac{5}{7}$$

$$R_T = \frac{5}{7} + 2 = \frac{20}{7}$$


$$I_s = \frac{20}{\frac{20}{7}} = 7A$$

Current division

$$I_{6\Omega} = 7 \cdot \frac{1}{1+3+3} = 1A$$

$$V_{AB} = V_{th} = I \cdot 3 = 1 \times 3 = 3V$$


R_{th}

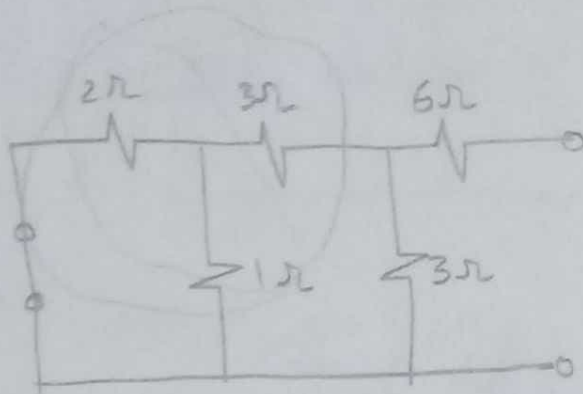

$$\frac{2 \times 1}{3} + 3 = \frac{11}{3}$$


$$\frac{\frac{11}{3} \times 3}{\frac{11}{3} + 3} = \frac{11 \times 3}{20} = \frac{33}{20}$$
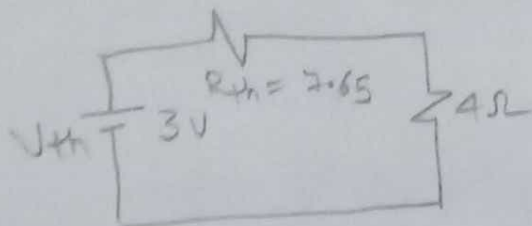
$$R_{th} = \frac{33}{20} + 6 = \frac{153}{20} = 7.65\Omega$$



$$I = \frac{3}{7.65 + 4} = 0.257A$$

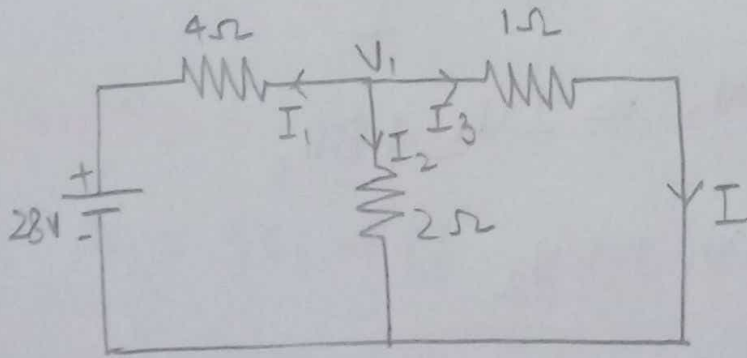2. Prove reciprocity theorem for the given circuit



Sol Case ① Apply KCL at node ①

$$\frac{V_1 - 28}{4} + \frac{V_1}{2} + \frac{V_1}{1} = 0$$

$$V_1 - 28 + 2V_1 + 4V_1 = 0$$

$$7V_1 = 28$$


$$V_1 = 28/7$$

$$V_1 = 4V$$

$$I = \frac{V_1}{1}$$

$$I = \frac{4}{1} = 4A //$$

Case ②

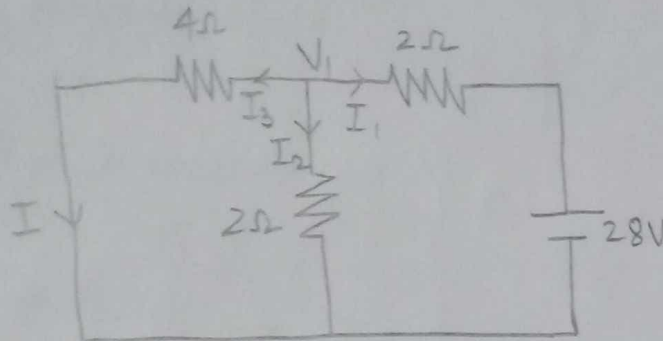

$$\frac{V_1 - 28}{1} + \frac{V_1}{2} + \frac{V_1}{4} = 0$$

$$4V_1 - 112 + 2V_1 + V_1 = 0$$

$$7V_1 = 112$$

$$V_1 = \frac{112}{7} = 16V$$

$$V_1 = 16V //$$


$$I = \frac{V}{R} = \frac{16}{4}$$

$$I = 4A //$$

$$\therefore \frac{V_a}{i_b} = \frac{V_a}{i_b} // \therefore \text{Hence reciprocity is verified}$$

$$\therefore \frac{28}{4} = \frac{28}{4} //$$

Average Value of AC Voltage

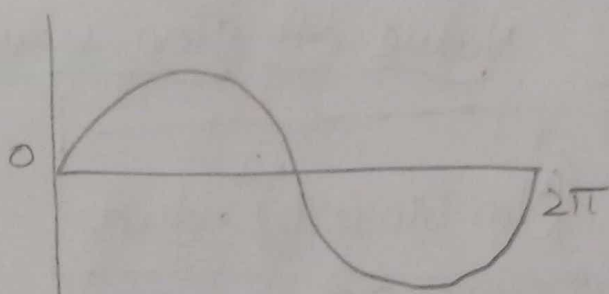

$$V_{avg} = \frac{1}{T} \int_0^T V_m \sin \omega t \cdot d\omega t$$

(or)

Time period = 2π $\rightarrow V_{avg} = \frac{\text{Total Area}}{2\pi} = 0$

$$V_{avg} = \frac{1}{2\pi} \int_0^{2\pi} V_m \sin \omega t \cdot d\omega t$$

complete
For \uparrow Sine Wave form, $V_{avg} = 0$

Therefore, consider average value of one half cycle.

$$V_{avg} = \frac{1}{T/2} \int_0^{T/2} V_m \sin \omega t \cdot d\omega t$$

$$V_{avg} = \frac{1}{\pi} \int_0^{\pi} V_m \sin \omega t \cdot d\omega t$$

$$V_{avg} = \frac{V_m}{\pi} [-\cos \omega t]_0^{\pi}$$

$$V_{avg} = -\frac{V_m}{\pi} [\cos \pi - \cos 0]$$

$$V_{avg} = -\frac{V_m}{\pi} [-1 - 1]$$

$$V_{avg} = -\frac{V_m}{\pi} (-2)$$

$$V_{avg} = \frac{2V_m}{\pi}$$

Root Mean Square Value of Sine wave form

$$V_{rms} = \sqrt{\frac{1}{T} \int_0^T (V_m \sin \omega t)^2 \cdot d\omega t}$$

$$= \sqrt{\frac{1}{2\pi} \int_0^{2\pi} V_m \left(\frac{1 - \cos 2\omega t}{2} \right) d\omega t} \quad \begin{cases} \cos 2\omega t = 1 - 2\sin^2 \omega t \\ \sin^2 \omega t = \frac{1 - \cos 2\omega t}{2} \end{cases}$$

$$V_{rms} = \sqrt{\frac{V_m^2}{4\pi} \int_0^{2\pi} (1 - \cos 2\omega t) d\omega t}$$


$$= \sqrt{\frac{V_m^2}{4\pi} \left[\omega t - \frac{\sin 2\omega t}{2} \right]_0^{2\pi}}$$

$$= \sqrt{\frac{V_m^2}{\frac{2\pi^2}{2}}} = \frac{V_m}{\sqrt{2}}$$

$$V_{rms} = \frac{V_m}{\sqrt{2}}$$

* Mid

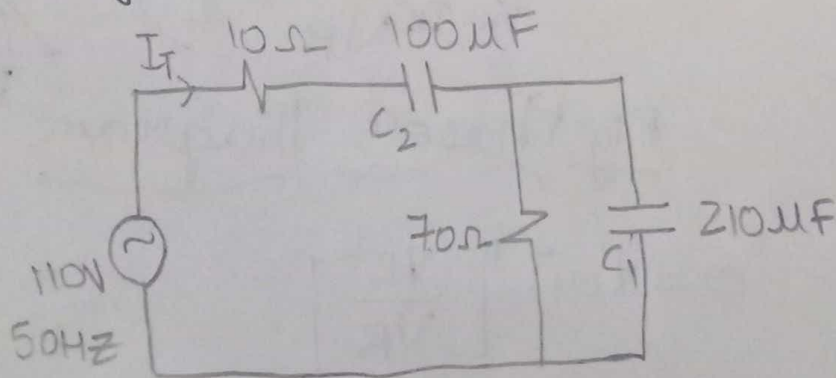1. Determine total impedance, total current, Phase angle for the circuit shown below.



Sol:

$$V_{rms} = 10V$$

$$f = 50Hz$$

$$X_{C1} = \frac{-j}{\omega C_1}$$


$$= \frac{-j}{2\pi(50) 210 \times 10^{-6}}$$

$$= \frac{-j10^6}{314 \times 210} = -j15.16 \Omega$$

$$X_{C2} = \frac{-j}{\omega C_2}$$

$$= \frac{-j}{2\pi(50) 100 \times 10^{-6}}$$
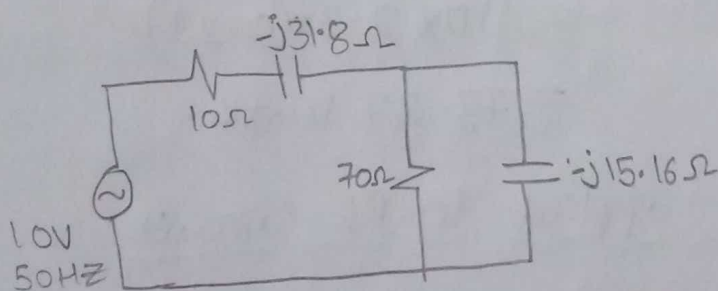
$$= \frac{-j \times 10^6}{2\pi(50) \times 100} = -j31.8 \Omega$$



$$Z_2 = \frac{70 \times -j15.16}{70 - j15.16}$$

$$Z_2 = \frac{70 \times 15.16 \angle -90^\circ}{\sqrt{70^2 + 15.16^2} \angle \tan^{-1}\left(\frac{-15.16}{70}\right)}$$

$$Z_2 = 14.81 \angle -90^\circ + 12$$

$$Z_2 = 14.81 \angle -78^\circ \rightarrow \text{Polar}$$

$$Z_2 = 14.81 \cdot \cos 78^\circ - j14.81 \sin 78^\circ$$

$$Z_2 = 3.06 - j14.48$$

$$Z_1 = \underline{\underline{10 - j31.8}}$$

$$Z_T = Z_1 + Z_2$$

$$= 10 - j31.8 + 3.06 - j14.48$$

$$= 13.06 - j45.54$$

$$= \sqrt{13.06^2 + 45.5^2} \angle -\tan^{-1}(\quad) = 47.3 \angle -73^\circ$$

$$I_T = \frac{110}{47.3 \angle -73^\circ} = 2.3 \angle 73^\circ$$

Phase angle $\theta = 73^\circ$ leading

$$\text{Power factor} = \cos \theta$$


$$= \cos 73^\circ = 0.29 \text{ leading}$$

$$\text{Active power} = VI \cos \theta$$


$$= 110 \times 2.3 \times (0.29)$$

$$= 73.37 \text{ Watts.}$$

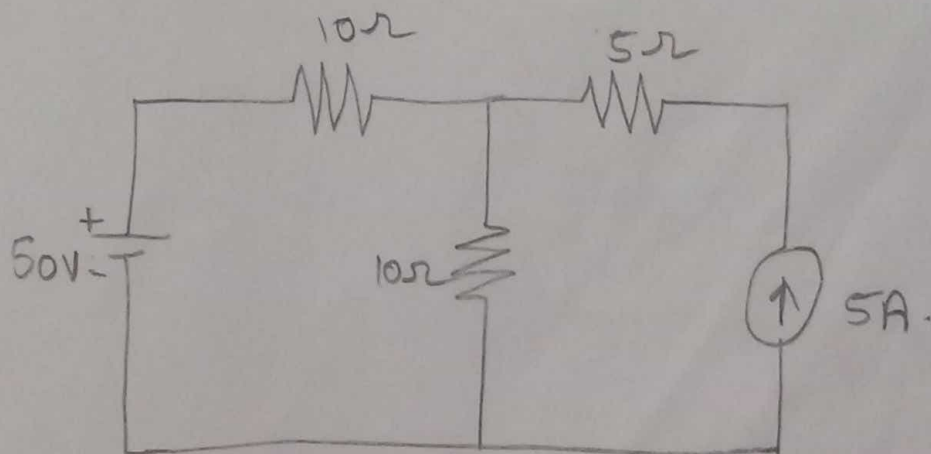2. Find current through 5Ω resistor using super position theorem.



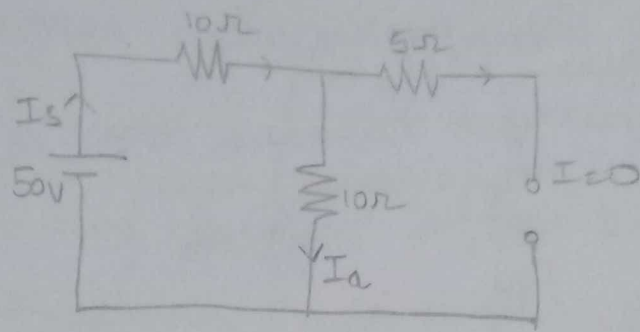
Sol (case i) While 50V source acting alone



$$I_s = \frac{50}{10+10} = 2.5A //$$

$$I_a = 2.5A //$$

(Case ii) while 5A source acting alone

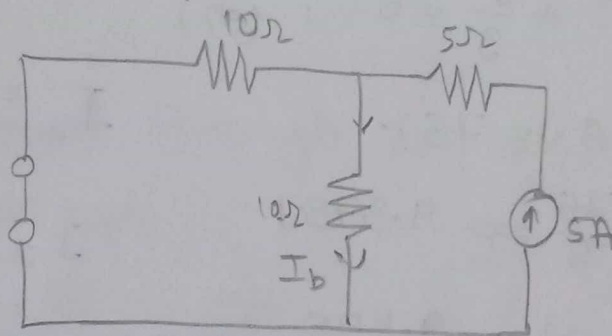

$$I_b = \frac{5 \cdot 10}{10+10} = 2.5A$$

$$I_1 = I_a + I_b$$

$$I_1 = 5A //$$

find current in various branches

$$I_{5A} = 5A //$$

Emf equation of Transformer

$$\text{let } \phi = \phi_m \sin \omega t$$

According to Faraday's law

$$\text{(Induced emf)} \quad E = \frac{-N d\phi}{dt}$$

$$E = \frac{-N d\phi_m \sin \omega t}{dt}$$

$$\text{(Instantaneous Induced emf)} \quad E = -N \omega \phi_m \cos \omega t$$

$$E = N \omega \phi_m \sin(\omega t - \pi/2) = E_m \sin(\omega t - \pi/2)$$

$$\text{For RMS Induced EMF} = \frac{N \omega \phi_m}{\sqrt{2}}$$

$$= \cancel{N 2\pi f} \frac{N 2\pi f \phi_m}{\sqrt{2}}$$

$$E_{rms} = 4.44 f \phi_m N_1 \Rightarrow E_1$$

$$E_{2rms} = 4.44 f \phi_m N_2 \Rightarrow E_2$$

$$\boxed{\frac{E_1}{E_2} = \frac{N_1}{N_2}}$$